

Voltaje en fuente	Voltaje en resistor	Voltaje en diodo	Corriente en diodo y resistor
0.1V	0	99.78mV	0
0.2V	0	200.2mV	0
0.3V	0	360.19mV	0
0.4V	0	405.1mV	0
0.5V	0	434.01mV	0
0.6V	0.148V	.57V	.67272mA
0.7V	0.208V	0.585V	.94545mA
0.8V	0.305V	0.606V	1.38mA
0.9V	0.397V	0.619V	1.804mA
1V	0.447V	0.625V	2.0318mA
1.5V	0.910V	0.659V	4.136mA
2V	1.409V	0.680V	6.404mA
2.5V	1.885V	0.694V	8.568mA
3V	2.375V	0.704V	10.795mA
5V	4.370V	0.751V	19.863mA

Practica 1 - Curva I-V del Diodo

Grafica obtenida a partir de los datos experimentales del archivo proporcionado.

